

## Question 8

With the aid of a sketch show how a PV array is linked using a grid tied inverter to the consumer's metering and electricity retailers' grid.

The sketch must include PV array, DC grid tied inverter, isolation from panels and on grid side of the grid tied inverter.